



# Digital Systems Review



Tran Ngoc Thinh

HCMC University of Technology

<http://www.cse.hcmut.edu.vn/~tnthinh>

## Kmap

- The minimum SOP

$$F(D, C, B, A) = \sum (0, 1, 2, 4, 5, 7, 9, 12) + \sum d(10, 11, 14, 15)$$

- a)  $D'B' + C'BA' + DC'A + D'CA$
- b)  $D'B' + DB + C'BA' + DC'A + D'CA + DCA'$
- c)  $C'BA' + CB'A' + D'CA + C'B'A$
- d)  $D'B' + C'BA' + DCA' + DC'A + D'CA$
- e)  $CB'A' + C'B'A + D'CA + D'C'A'$

## Boolean Algebra

- Find the SOP minimum form :
  - $F(DCBA) = \sum(0,1,2,8,11,12) + d(3,9,13)$ 
    - A.  $A'B' + A'C' + B'D$
    - B.  $D'C' + DB' + C'A$
    - C.  $D'C + DB + C'A$
  - $X = B(A+C) + C((AB)'.A)'$ 
    - A.  $F = A'C + BC$
    - B.  $F = AB + A'C$
    - C.  $F = ABC + A'C$
    - D.  $F = AB + BC + A'C$
    - E.  $F = 1$

## Boolean Algebra

1) Choose a FALSE statement:

- a) An AND gate can be used as a merging circuit
- b) A NOR gate can be used as a enable/disable circuit
- c) A XNOR gate can be used as a selectable inversion circuit
- d) All above statements are FALSE

2) Convert these numbers:  $275_{10}$  and  $641_{10}$  into BCD format and perform a BCD addition.

- a)  $100010110110_{BCD}$
- b)  $100110110110_{BCD}$
- c)  $100100010110_{BCD}$
- d)  $100100010100_{BCD}$

## Design

- A combinational circuit with 4 inputs A, B, C, D and 1 output X. Output  $X = A'$  when and only if B, C are at level 0 (LOW) or  $C=D$ . With remaining cases, output  $X = 0$ . The Boolean algebra for the output X is:

- a)  $A'.(B.C + C'.D' + C.D)'$
- b)  $A'.(B'.C' + C'.D' + C.D)$
- c)  $A' + (B' + C').(C'.D' + C.D)$
- d)  $A' + (B'.C' + (C \oplus D))$
- e)  $A'.(B.C + (C \oplus D)')$




## Arithmetic

- The fast carry or look-ahead carry circuits found in most 4-bit parallel-adder circuits
  - add a 1 to complemented inputs
  - increase ripple delay
  - reduce propagation delay
  - determine sign and magnitude
- How many bits would be required to represent decimal numbers from -32,768 to + 32,767?
  - 16
  - 15
  - 14
  - 13




## Counter 74293 (1)

 


- Determine the frequency at Q3 of U2, Given  $f_{CLK} = 100$  KHz
  - 6.25 KHz
  - $\approx 7.14$  KHz
  - $\approx 3.57$  KHz
  - 3.125 KHz
  - 1.5625 KHz

## Counter 74293 (2)

 


- Assume that the initial value of the counter  $Q_3Q_2Q_1Q_0$  (U1) = 0011 and  $Q_3Q_2Q_1Q_0$  (U2) = 1100. Determine the state of  $Q_3Q_2Q_1Q_0$  (U2) after next 5 clock cycles of CLK.
  - 0000
  - 1110
  - 0111
  - 1101

## Counter 74293 (3)

 

- Determine MOD of the counter
  - A. 8
  - B. 16
  - C. 32
  - D. 56
  - E. 64

## Counter

 

- MOD?
- 40
- 45
- 50
- 90

MODE SELECT TABLE

MR	PL	CP <sub>U</sub>	CP <sub>D</sub>	MODE
H	X	X	X	Reset (Asyn.)
L	L	X	X	Preset (Asyn.)
L	H	H	H	No Change
L	H	H	H	Count Up
L	H	H	$\bar{H}$	Count Down

# Registers

1. In contrast to a binary counter, how many extra Flip-Flops does a ring counter use if both counters are MOD-8?
  - a. 3
  - b. 4
  - c. 5
  - d. 6
2. In contrast to a binary counter, how many extra Flip-Flops does a Johnson counter use if both counters are MOD-8?
  - a) 4
  - b) 3
  - c) 2
  - d) 1




# Registers

1. Given 8-bit shift register X = 10101111 and Data input at HIGH(1) connected with MSB bit, after shift right 6 clock cycles, the value of register X is:
  - a. 10101111
  - b. 11111110
  - c. 11101011
  - d. 11111111
2. Given 8-bit shift register X = 10101111 and 8-bit shift register Y = 00000000, MSB bit of X connects with LSB bit of Y. After shift left six(6) clock cycles, the value of register Y is:
  - a) 10101111
  - b) 10111100
  - c) 00101011
  - d) 11101011


 
## Timing diagram

- Sketch a timing diagram showing the waveforms of Qa, Qb, Qc and Qd as following circuit. Note that CP (clock), S (preset), R (reset).



## MSI Circuits

**1) What are the outputs of a 7485 four-bit magnitude comparator when the inputs are A = 0001 and B = 0100?**

- A) A < B is 0 A = B is 1 A > B is 1
- B) A < B is 0 A = B is 1 A > B is 0
- C) A < B is 1 A = B is 0 A > B is 0
- D) A < B is 0 A = B is 0 A > B is 1

**2) Which device is used in computer hardware to interpret the binary code of the computer instruction?**

- A) decoder
- B) multiplexer
- C) encoder
- D) demultiplexer

## Design

- Construct an 8-to-1 MUX using any number of 4-to-1 and 2-to-1 MUXs as building blocks. Use the smallest number of component MUXs that you can.
- .

## Decoder Example (1)

- Draw the diagram to show how to realize the functions  $F(W,X,Y) = \Sigma(1,3,5,6)$  and  $G(W,X,Y) = \Sigma(2,3,4,7)$  using only a single 74LS138 and two NAND gates.
- .



## Decoder Example (2)

- Draw the diagram to show how to realize the functions  $F(A,B,C,D) = \Sigma(2,4,6,14)$  using only one 74LS138 and one NAND gates.

## MUX Example (1)

- Draw the diagram to show how to realize the functions  $F(W,X,Y) = \Pi(3,4,5,6,7)$  using only a 74LS151.
-

## MUX Example (2)

- Draw the diagram to show how to realize the functions  $F(A,B,C,D) = \Sigma(2,4,6,14)$  using only a 74LS151.
- 

## MUX homework

- Draw the diagram to show how to realize the functions  $F(A,B,C,D) = \Sigma(1,5,7,8,9,13,14)$  (with B, C, and D as the control inputs) using only a 74LS151.